

# Code Structure

## Library, Entity, Architecture

*Definition, operators, functions, procedures components,  
constans, types.*

**VHDL**  
**VHSIC HARDWARE**  
**DESCRIPTION LANGUAGE**


## Code Structure Design Flow

```
-----  
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
-----
```

```
ENTITY full_adder IS  
PORT (a, b, cin: IN BIT;  
s, cout: OUT BIT);  
END full_adder;  
-----
```


```
ARCHITECTURE dataflow OF full_adder IS  
BEGIN  
s <= a XOR b XOR cin;  
cout <= (a AND b) OR (a AND cin) OR  
        (b AND cin);  
END dataflow;
```

 - A minimum standalone code of VHDL is composed of **Library**, **Entity** and **Architecture**.
  - **LIBRARY** declarations: Contains a list of all libraries to be used in the design.
  - **ENTITY**: Specifies the I/O pins of the circuit.
  - **ARCHITECTURE**: Contains the VHDL code proper, which describes how the circuit should behave (function).



# Code Structure

## Library

 

A **Library** is structured based on Functions, procedures or components which are placed inside **PACKAGES** and then compiled into the destination library.

**LIBRARY** declarations: Contains a list of all libraries to be used in the design.

Syntax:

```
LIBRARY library_name;  
USE library_name.package_name.package_parts;
```

Libraries usually required:

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;
```

-- A semi-colon (;) indicates  
-- the end of a statement or


```
LIBRARY std;  
USE std.standard.all;
```

-- declaration, while a double  
-- dash (--) indicates a comment.

```
LIBRARY work;  
USE work.all;
```

Note that libraries *std* and *work* are available by default and therefore there is no need to declare them.

## Code Structure Library

 



A **Library** is structured based on Functions, procedures or components which are placed inside **PACKAGES** and then compiled into the destination library.

- **std** is a resource library (data types, text i/o, etc.) for the VHDL design environment;
- **work** library is where we save our design (the .vhd file, plus all files created by the compiler, simulator, etc.)

In addition, we have several packages from ieee library as:

- **std\_logic\_1164**: Specifies a multi-level logic system. The STD\_LOGIC (8 levels) and STD\_ULOGIC (9 levels) multi-valued logic systems.
- **std\_logic\_arith**: Specifies the SIGNED and UNSIGNED data types and related arithmetic and comparison operations. It also contains several data conversion functions, which allow one type to be converted into another: conv\_integer(p), conv\_unsigned(p, b), conv\_signed(p, b), conv\_std\_logic\_vector(p, b).
- **std\_logic\_signed**: Contains functions that allow operations with STD\_LOGIC\_VECTOR data to be performed as if the data were of type SIGNED.
- **std\_logic\_unsigned**: Contains functions that allow operations with STD\_LOGIC\_VECTOR data to be performed as if the data were of type UNSIGNED

## Code Structure Entity

  

```
ENTITY nand_gate IS
  PORT (a, b : IN BIT;
        x : OUT BIT);
END nand_gate;
```

**ENTITY** is a list with specifications of all input and output pins (PORTS) of the circuit.

Syntax:

```
ENTITY entity_name IS
  PORT (
    port_name : signal_mode signal_type;
    port_name : signal_mode signal_type;
    ...);
END entity_name;
```

**Signal Mode** can be IN, OUT, INOUT (bidirectional) or BUFFER (for output signals that are used (read) internally).


**Signal Type** can be BIT, STD\_LOGIC, INTEGER, etc. (we see this later).

**Entity Name** can be any name, except VHDL. It is the name of your entity **and .vhd file**


 
## Code Structure Architecture

**ARCHITECTURE** is the description of the functionality of the circuit.  
Syntax (it has two parts, declarations and code)



```
ARCHITECTURE architecture_name OF entity_name IS  
[declarations]  
BEGIN  
(code)  
END architecture_name;
```

- The declarative part (optional) declares signals and constants (among others).
- The code part define the function of the code.

```
ARCHITECTURE myarch OF nand_gate IS  
BEGIN  
    x <= a NAND b;  
END myarch;
```

'<='Assign the result of "a AND b" to x.

There are three different modelling styles for architecture body:

**Data flow** : The circuit is described using concurrent statements

**Behavioral** : The circuit is described using sequential statements


**Structural** : The circuit is described using different interconnected components

Mixed style is also allowed, using two or the three styles.

## Code Structure
 
### Exercises –FlipFlop Source Code

Implement a D-type flip-flop (DFF) and simulate its behavior to validate its code.



- The flip-flop is triggered at rising Edge of the clock signal clk
- It possesses an asynchronous reset
- If reset is high, output must be low regardless of clk.
- If reset is low, the input d is copied to the output q at the clock raising

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity Class_VHDL_Exercise_1 is
    Port ( d, clk, rst : in STD_LOGIC;
          q : out STD_LOGIC);
end Class_VHDL_Exercise_1;


architecture Behavioral of Class_VHDL_Exercise_1 is
begin
    PROCESS (rst, clk)
    BEGIN
        IF(rst='1') THEN
            q <= '0';
        ELSIF (clk'EVENT AND clk='1') THEN
            q <= d;
        END IF;
    END PROCESS;
end Behavioral;
```

## Code Structure
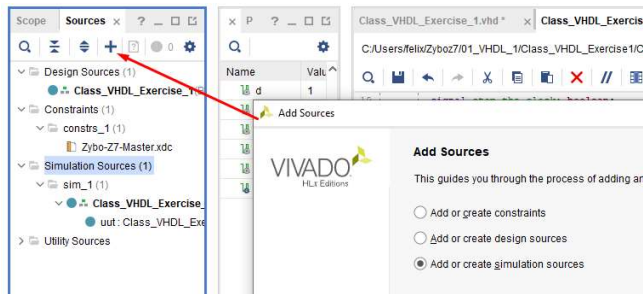
### Exercises-FlipFlop Test Bench For Simulation

In order to simulate our design, we need to create a simulation testbench.

For doing that, we need to add a new simulation source here:



Once created, you need to copy the text on the right. That will create the environment and conditions of the simulation.

For creating the code use this [website](#).

A future complete lecture will be dedicated to create testbenchs!  
No worries for now.

```
library IEEE;
use IEEE.Std_logic_1164.all;
use IEEE.Numeric_Std.all;

entity Class_VHDL_Exercise_1_tb is
end;

architecture bench of Class_VHDL_Exercise_1_tb is

    component Class_VHDL_Exercise_1
        Port ( d, clk, rst : in STD_LOGIC;
              q : out STD_LOGIC);
    end component;

    signal d, clk, rst: STD_LOGIC;
    signal q: STD_LOGIC;

    constant clock_period: time := 10 ns;
    signal stop_the_clock: boolean;

begin

    uut: Class_VHDL_Exercise_1 port map ( d  => d,
                                           clk => clk,
                                           rst => rst,
                                           q  => q );

    stimulus: process
    begin

        -- Put initialisation code here
        d<='1';
        wait for 50 ns;
        d<='1';
        wait for 50 ns;
        -- Put test bench stimulus code here
        stop_the_clock <= true;
        wait;
        end process;

    clocking: process
    begin
        while not stop_the_clock loop
            clk <= '0', '1' after clock_period / 2;
            wait for clock_period;
        end loop;
        wait;
        end process;


end;
```



# Code Structure

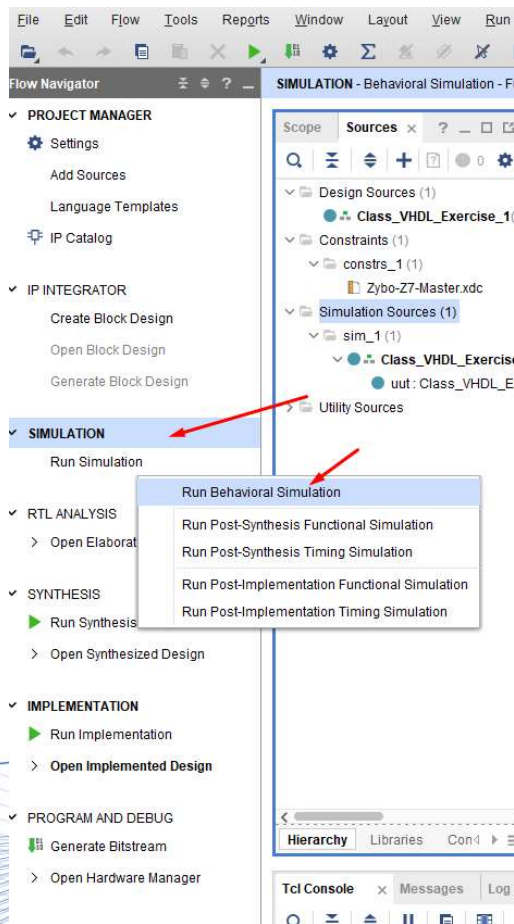
## Exercises-Simulation

Once the simulation file is ready, we can run the simulation:



```
stimulus: process
begin

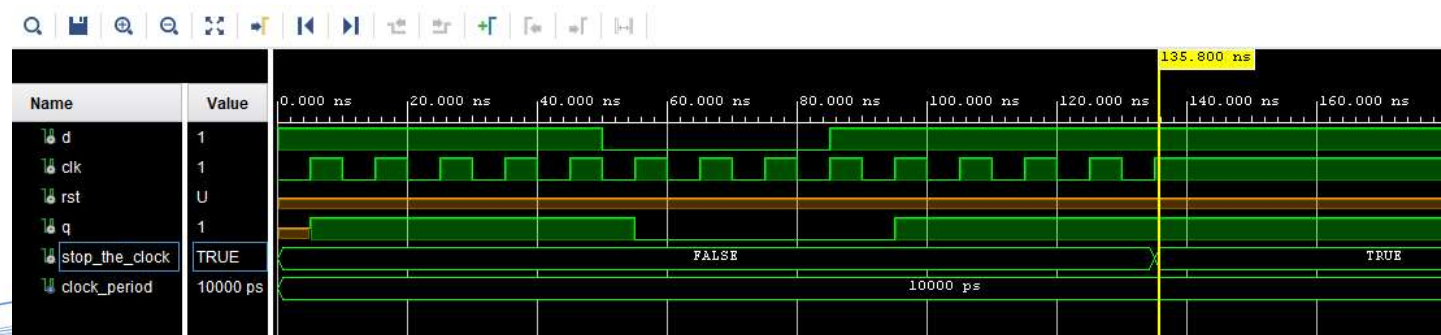    -- Put initialisation code here
    d<='1';
    wait for 50 ns;
    d<='0';
    wait for 35 ns;
    d<='1';
    wait for 50 ns;
    -- Put test bench stimulus code here
    stop_the_clock <= true;
    wait;
end process;
```



# END-Code Structure

## Library, Entity, Architecture

*Definition, operators, functions, procedures components,  
constans, types.*

**VHDL**  
**VHSIC HARDWARE**  
**DESCRIPTION LANGUAGE**