

State Machines


Modeling Sequential Logic Circuits

Finite State Machines - FSM

VHDL
VHSIC HARDWARE
DESCRIPTION LANGUAGE

State Machines

Definition Finite State Machines (FSM)

 


- Figure shows a single-phase State machine.
- Combinational and sequential logic (C.L. and S.L.) are well differentiated.
- C.L. has 2 inputs and 2 output.
- S.L. has 3 inputs and one output.
- S.L. contains the flip-flops and is designed by PROCESS.
- C.L. can be designed with or without PROCESS. (designer definition)
- **Clock** and **Reset** are usually in sensitivity list of PROCESS. So, they are in S.L.
- If output of FSM depends on current state and its input -> **Mealy** machine.
- If output of FSM depends only on current state -> **Moore** machine.
- Although any circuit can be design as FSM, we only use this approach for **systems whose task are clearly a list of different states**. E.g., traffic light.

State Machines

Designing FSM – Template Style 1 (no stored output)

```
PROCESS (input, pr_state)
BEGIN
  CASE pr_state IS
    WHEN state0 =>
      IF (input = ...) THEN
        output <= <value>;
        nx_state <= state1;
      ELSE ...
      END IF;
    WHEN state1 =>
      IF (input = ...) THEN
        output <= <value>;
        nx_state <= state2;
      ELSE ...
      END IF;
    WHEN state2 =>
      IF (input = ...) THEN
        output <= <value>;
        nx_state <= state2;
      ELSE ...
      END IF;
    ...
  END CASE;
END PROCESS;
```
 
```
PROCESS (reset, clock)
BEGIN
  IF (reset='1') THEN
    pr_state <= state0;
  ELSIF (clock'EVENT AND clock='1') THEN
    pr_state <= nx_state;
  END IF;
END PROCESS;
```



S.L Part:


- Is made based on PROCESS
- Reset is asynchronous and set “state 0” to present state (pr_state).
- Next State (nx_state) is assigned synchronously.
- Number of flip-flops (n) is equal to the number of bits (n) used to encode all states (S). $2^n = S$; $n = \log_2(S)$.

C.L Part:

- Sequential code is selected using CASE statement.
- The code assign output value
- It establishes next state.
- Rules of design of C.L. circuits are fulfilled:
 - Rule1: All input/output combinations are specified.
 - Rule2: Sequential statements are present for all signals of sensitivity list.

State Machines

 Designing FSM – Template Style 1 (no stored ou



This is how the template for a full code of FSM looks:

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;



-----
ENTITY <entity_name> IS
    PORT ( input: IN <data_type>;
          reset, clock: IN STD_LOGIC;
          output: OUT <data_type>);
END <entity_name>;
-----
ARCHITECTURE <arch_name> OF <entity_name> IS
    TYPE state IS (state0, state1, state2, state3, ...);
    SIGNAL pr_state, nx_state: state;
BEGIN
    ----- Lower section: -----
    PROCESS (reset, clock)
    BEGIN
        IF (reset='1') THEN
            pr_state <= state0;
        ELSIF (clock'EVENT AND clock='1') THEN
            pr_state <= nx_state;
        END IF;
    END PROCESS;
    ----- Upper section: -----
    PROCESS (input, pr_state)
    BEGIN
        CASE pr_state IS
            WHEN state0 =>
                IF (input = ...) THEN
                    output <= <value>;
                    nx_state <= state1;
                ELSE ...
                END IF;
            WHEN state1 =>
                IF (input = ...) THEN
                    output <= <value>;
                    nx_state <= state2;
                ELSE ...
                END IF;
            WHEN state2 =>
                IF (input = ...) THEN
                    output <= <value>;
                    nx_state <= state3;
                ELSE ...
                END IF;
            ...
        END CASE;
    END PROCESS;
END <arch_name>;
```


State Machines

  Example Moore Machine

A counter is a circuit which next state only depends on its present state. (moore).

It can be implemented as FSM (not Good idea) or conventionally with arithmetic operations as seen before (better idea).



```

-----
LIBRARY ieee;
USE ieee.std_logic_1164.all;
-----

ENTITY counter IS
    PORT ( clk, rst: IN STD_LOGIC;
          count: OUT STD_LOGIC_VECTOR (3 DOWNT0 0));
END counter;
-----

ARCHITECTURE state_machine OF counter IS
    TYPE state IS (zero, one, two, three, four,
                  five, six, seven, eight, nine);
    SIGNAL pr_state, nx_state: state;
BEGIN
    ----- Lower section: -----
    PROCESS (rst, clk)
    BEGIN
        IF (rst='1') THEN
            pr_state <= zero;
        ELSIF (clk'EVENT AND clk='1') THEN
            pr_state <= nx_state;
        END IF;
    END PROCESS;
    ----- Upper section: -----
    PROCESS (pr_state)
    BEGIN
        CASE pr_state IS
            WHEN zero =>
                count <= "0000";
                nx_state <= one;
            WHEN one =>
                count <= "0001";
                nx_state <= two;

```

```

            WHEN two =>
                count <= "0010";
                nx_state <= three;
            WHEN three =>
                count <= "0011";
                nx_state <= four;
            WHEN four =>
                count <= "0100";
                nx_state <= five;
            WHEN five =>
                count <= "0101";
                nx_state <= six;
            WHEN six =>
                count <= "0110";
                nx_state <= seven;
            WHEN seven =>
                count <= "0111";
                nx_state <= eight;
            WHEN eight =>
                count <= "1000";
                nx_state <= nine;
            WHEN nine =>
                count <= "1001";
                nx_state <= zero;
        END CASE;
    END PROCESS;
END state_machine;




```

State Machines

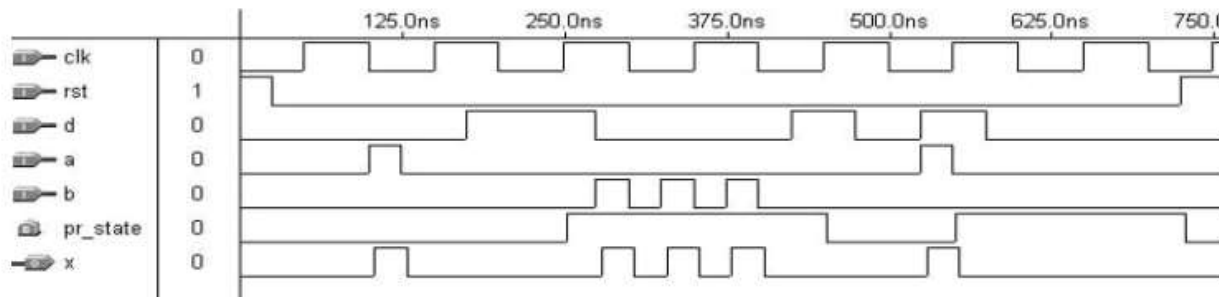  Example Mealy Machine

Suppose a circuit that has two states. It changes its state when an input d is equal to 1. Also, has two inputs, a and b , which is reflected to the output according to its state. As showed in this figure.

We can write this FSM using the same structure we have learned.




```

-----
ENTITY simple_fsm IS
    PORT ( a, b, d, clk, rst: IN BIT;
          x: OUT BIT);
END simple_fsm;
-----
ARCHITECTURE simple_fsm OF simple_fsm IS
    TYPE state IS (stateA, stateB);
    SIGNAL pr_state, nx_state: state;
BEGIN
    ----- Lower section: -----
    PROCESS (rst, clk)
    BEGIN
        IF (rst='1') THEN
            pr_state <= stateA;
        ELSIF (clk'EVENT AND clk='1') THEN
            pr_state <= nx_state;
        END IF;
    END PROCESS;
    ----- Upper section: -----
    PROCESS (a, b, d, pr_state)
    BEGIN
        CASE pr_state IS
            WHEN stateA =>
                x <= a;
                IF (d='1') THEN nx_state <= stateB;
                ELSE nx_state <= stateA;
                END IF;
            WHEN stateB =>
                x <= b;
                IF (d='1') THEN nx_state <= stateA;
                ELSE nx_state <= stateB;
                END IF;
        END CASE;
    END PROCESS;
END simple_fsm;
-----
    
```

State Machines


Designing FSM with Synchronous Output

 

So far, the output of our FSM changes asynchronously. Therefore, flip-flops are only on S.L. circuits.

If we need to **update the output synchronously** with a change in the input (synchronous Mealy machine), **output must be stored** as well.

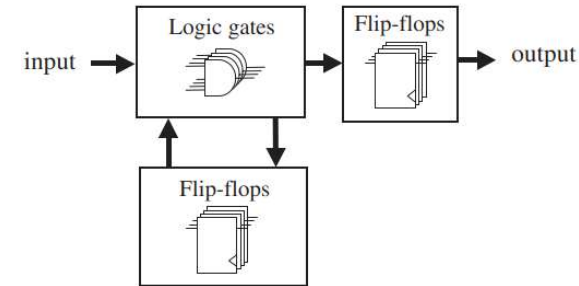Now **temp** is a signal, and the output is updated synchronously.



```

LIBRARY ieee;
USE ieee.std_logic_1164.all;

-----
ENTITY <ent_name> IS
    PORT (input: IN <data_type>;
          reset, clock: IN STD_LOGIC;
          output: OUT <data_type>);
END <ent_name>;

-----
ARCHITECTURE <arch_name> OF <ent_name> IS
    TYPE states IS (state0, state1, state2, state3, ...);
    SIGNAL pr_state, nx_state: states;
    SIGNAL temp: <data_type>;
BEGIN
    ----- Lower section: -----
    PROCESS (reset, clock)
    BEGIN
        IF (reset='1') THEN
            pr_state <= state0;
        ELSIF (clock'EVENT AND clock='1') THEN
            output <= temp;
            pr_state <= nx_state;
        END IF;
    END PROCESS;

```

```


----- Upper section: -----
PROCESS (pr_state)
BEGIN
    CASE pr_state IS
        WHEN state0 =>
            temp <= <value>;
            IF (condition) THEN nx_state <= state1;
            ...
        END IF;
        WHEN state1 =>
            temp <= <value>;
            IF (condition) THEN nx_state <= state2;
            ...
        END IF;
        WHEN state2 =>
            temp <= <value>;
            IF (condition) THEN nx_state <= state3;
            ...
        END IF;
        ...
    END CASE;
END PROCESS;
END <arch_name>;

```

State Machines

 Exercise

Generate a circuit that can output a signal as showed in the figure. You must use rising and falling edges of the clock to implement this clock divider (Hint: you can use two state machines , one for each edge and then AND them). The circuit has only clk as input. (output is obviously synchronous)



```

-----
ENTITY signal_gen IS
    PORT ( clk: IN BIT;
           outp: OUT BIT);
END signal_gen;
-----
ARCHITECTURE fsm OF signal_gen IS
    TYPE state IS (one, two, three);
    SIGNAL pr_statel, nx_statel: state;
    SIGNAL pr_state2, nx_state2: state;
    SIGNAL out1, out2: BIT;
BEGIN

    ----- Lower section of machine #1: ---
    PROCESS(clk)
    BEGIN
        IF (clk'EVENT AND clk='1') THEN
            pr_statel <= nx_statel;
        END IF;
    END PROCESS;

    ----- Lower section of machine #2: ---
    PROCESS(clk)
    BEGIN
        IF (clk'EVENT AND clk='0') THEN
            pr_state2 <= nx_state2;
        END IF;
    END PROCESS;

    ----- Upper section of machine #1: -----
    PROCESS (pr_statel)
    BEGIN
        CASE pr_statel IS
            WHEN one =>
                out1 <= '0';
                nx_statel <= two;
            WHEN two =>
                out1 <= '1';
                nx_statel <= three;
            WHEN three =>
                out1 <= '1';
                nx_statel <= one;
        END CASE;
    END PROCESS;

    ----- Upper section of machine #2: -----
    PROCESS (pr_state2)
    BEGIN
        CASE pr_state2 IS
            WHEN one =>
                out2 <= '1';
                nx_state2 <= two;
            WHEN two =>
                out2 <= '0';
                nx_state2 <= three;
            WHEN three =>
                out2 <= '1';
                nx_state2 <= one;
        END CASE;
    END PROCESS;

    outp <= out1 AND out2;
END fsm;
-----

```


Fixed Point Division

Exercise

Generate a circuit can make a generic division of two aleatory numbers a and b ($y=a/b$).

Remember that division operation “/” represent only a shift operation (equivalent to say that is a division by 2).

See this table to understand the algorithm required for division $11/3=3$ con resto 2:

Index (i)	a-related input (a_inp)	Comparison	b-related input (b_inp)	y (quotient)	Operation on 1 st column
3	1011	<	0011000	0	none
2	1011	<	0001100	0	none
1	1011	>	0000110	1	a_inp(i)-b_inp(i)
0	0101	>	0000011	1	a_inp(i)-b_inp(i)

0010 (rem)

a_inp

11

11

11

11-6=5

5-3=2

b_inp

24

12

6

3

a and **b** are of $n+1$ bits (e.g 4bits)
Extended **b** is of $2n+1$ bits (e.g. 7bits)
b is shifted in **i=n=3** positions.

$Y=0011=3$

Remainder: 0010=2.

END-State Machines

Modeling Sequential Logic Circuits

Finite State Machines - FSM

VHDL
VHSIC HARDWARE
DESCRIPTION LANGUAGE